

**A 1.4GHz 0.12pJ 4-bit  
Absolute-Value Detector for use  
in Neural Spike Sorting**

<b>Devyen Biswas,</b>	<b>804988161</b>
<b>Puvali Chatterjee,</b>	<b>504822474</b>
<b>Atharva Deo,</b>	<b>405350595</b>



# Design Summary

---


- **Mixed design with PTL and Static CMOS**
  - Reason: Minimum # of transistors, optimizes delay-energy metric
- **Stage 1 (absolute value calculation):**
  - $|X| + \sim T = |X| - T - 1 \leftarrow$  nonnegative if  $|X| > T$
  - MUX selector is  $X_3$ ; determines whether  $X$  is positive or negative then  $|X|$  is sent to stage 2
  - $T$  is inverted and sent to stage 2
- **Stage 2 (comparator):**
  - Optimized ripple-carry adder carry-out logic (using inversion property) with mirror adders to calculate 2<sup>nd</sup>-last  $C_{out}$  (i.e.  $C_2$ )
  - $C_{in} = X_3$
  - $C_2 = 1 \rightarrow |X| > T$
  - $C_2 = 0 \rightarrow |X| \leq T$


# Sizing and Optimization

---



- Unit inverter:  $w_p = 650 \text{ nm}$ ,  $w_n = 430 \text{ nm}$
- 0.5x inverter:  $w_p = 325 \text{ nm}$ ,  $w_n = 215 \text{ nm}$
- 4x inverter:  $w_p = 2.6 \text{ }\mu\text{m}$ ,  $w_n = 1.72 \text{ }\mu\text{m}$
- We initially tried logical effort sizing and using 0.5x inverters in the critical paths, 1x inverters in the non-critical paths and 4x inverter closest to the load
- We later found that using 0.5x inverters everywhere and a 4x inverter closest to output (to invert  $C_2$  from last mirror adder) offers the best balance of minimized delay and energy

# Full Absolute Value Detector


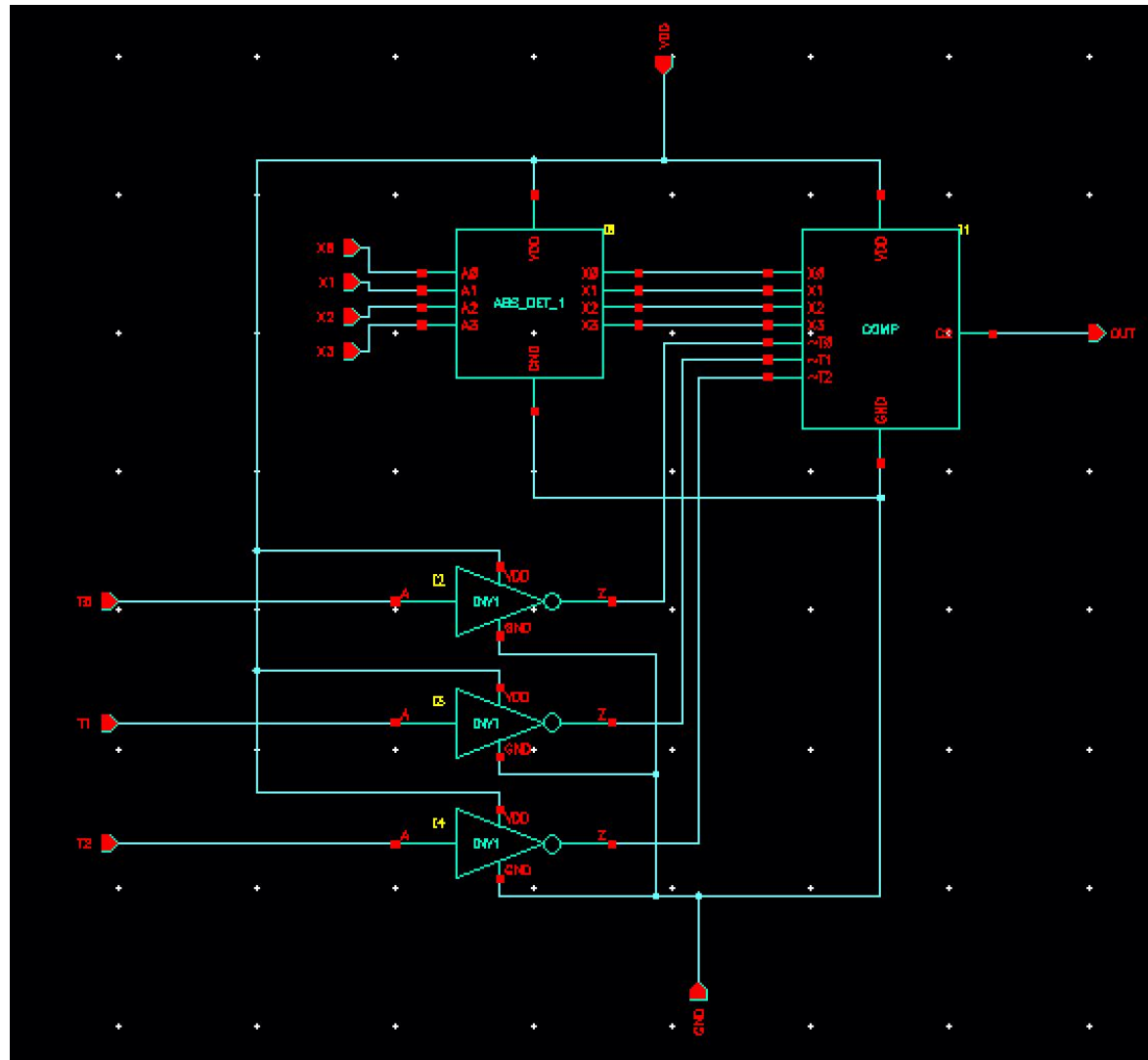


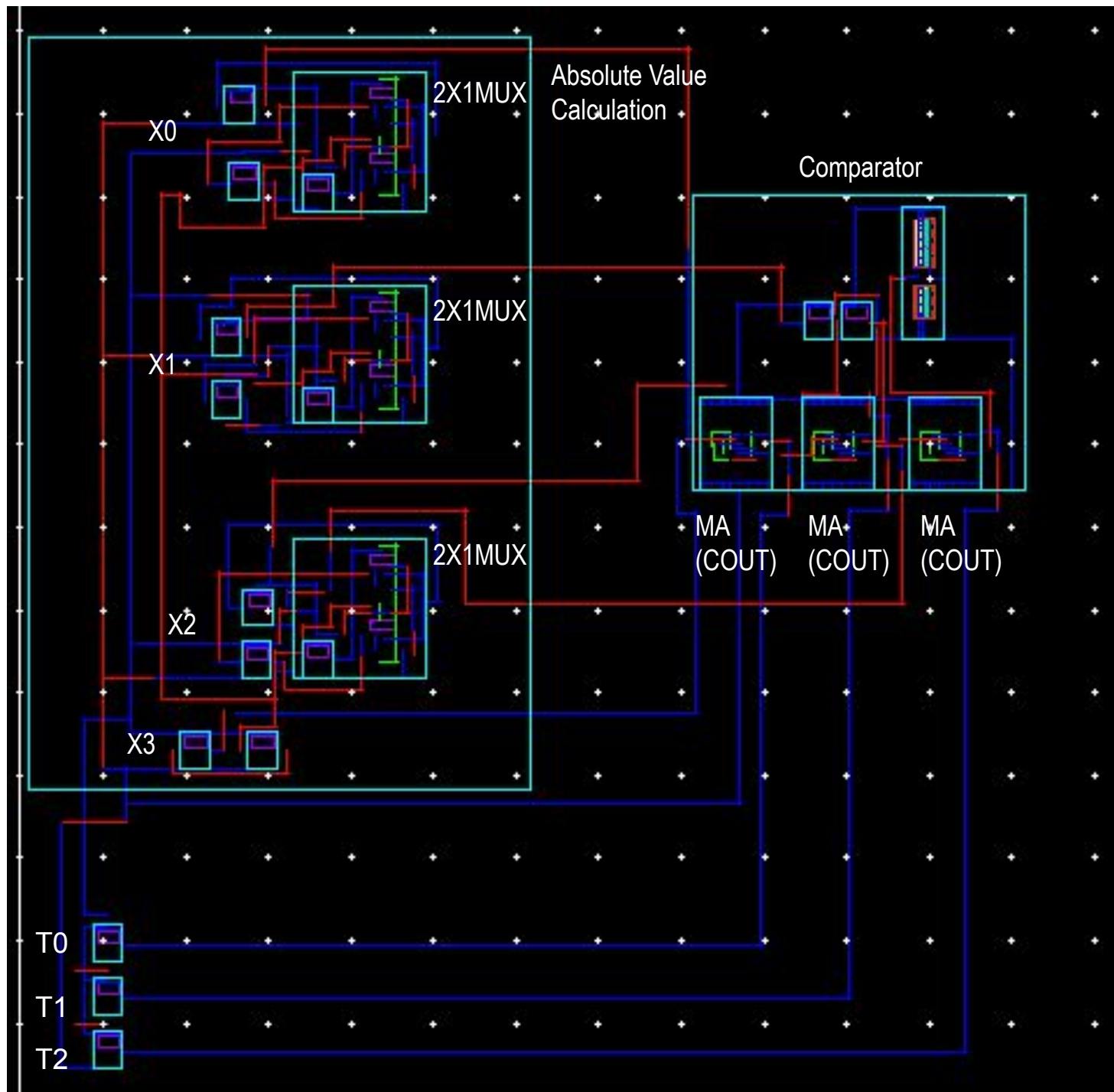

# Stage 1: Absolute Value Calculation

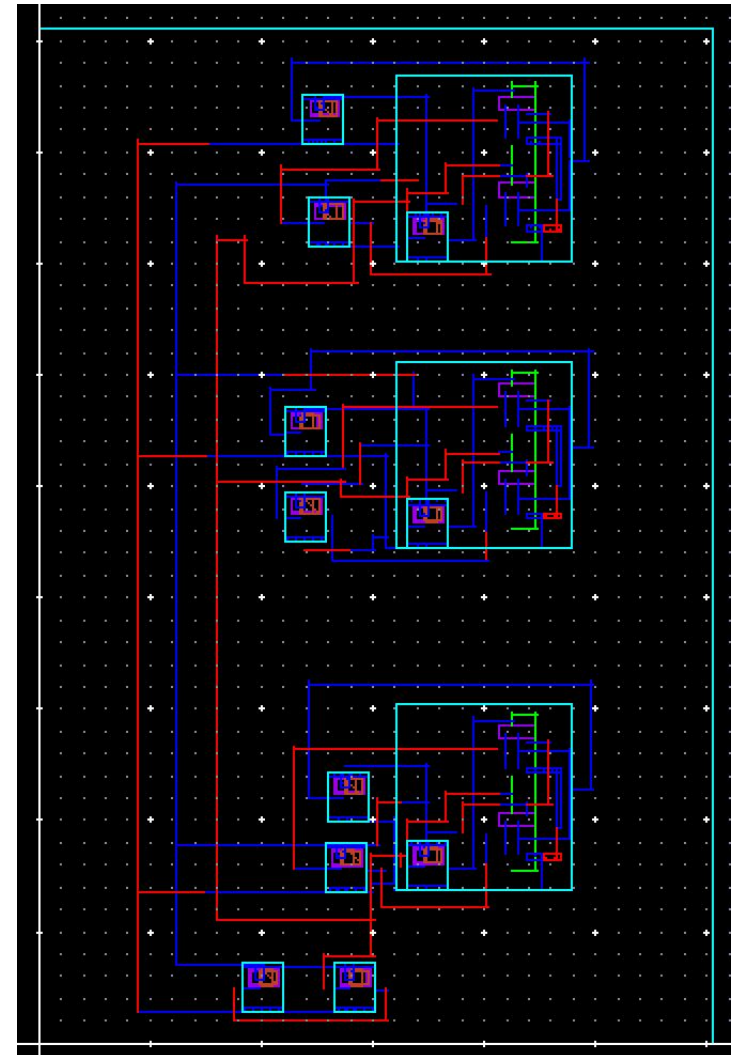
 


# Stage 2: Comparator

 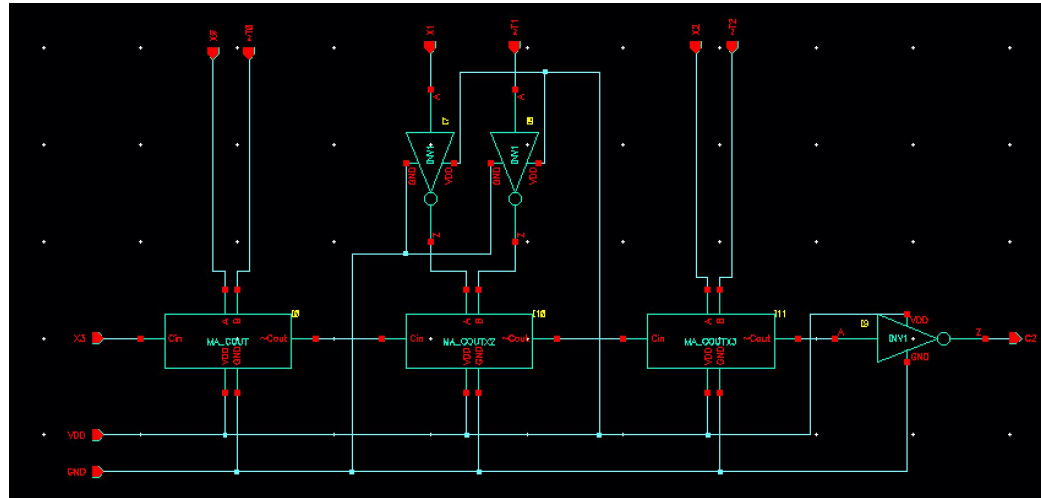





# Mirror Adder (carryout only)

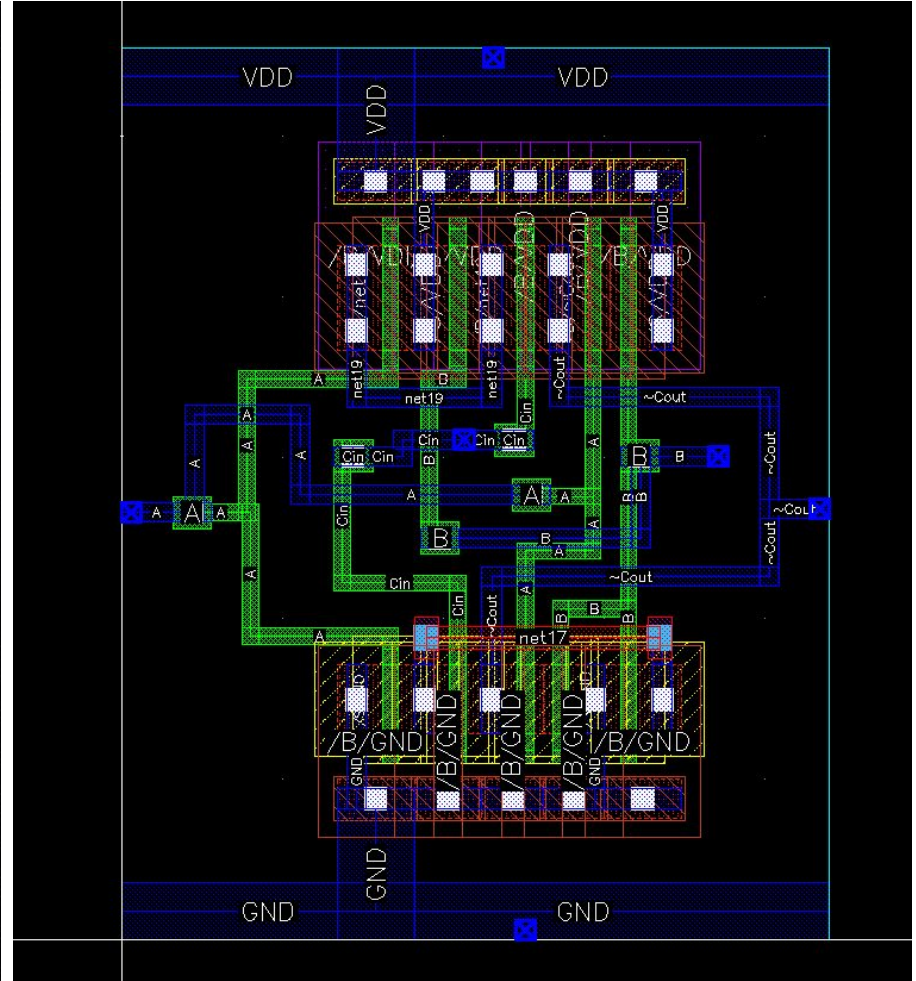
 






# Multiplexor (2X1MUX)

  

# 0.5X Inverter

  


# 4X Inverter

  

 
# Critical Path, Delay and Energy

- The input vectors associated with the 3 worst delay paths are  $X_0$ ,  $X_1$  and  $X_3$


$$- t_{\text{critical\_X0}} = 2t_{\text{INV\_0.5}} + t_{\text{TG}} + 3t_{\text{MA\_COUT}} + t_{\text{INV\_4}}$$


 
$$- t_{\text{critical\_X1}} = 3t_{\text{INV\_0.5}} + t_{\text{TG}} + 2t_{\text{MA\_COUT}} + t_{\text{INV\_4}}$$



 
$$- t_{\text{critical\_X3}} = 4t_{\text{INV\_0.5}} + 3t_{\text{MA\_COUT}} + t_{\text{INV\_4}}$$




- Final  $V_{\text{DD}}$  (post-layout): **674 mV**
- Minimum energy (post-layout): **205.15 fJ**
- **NOTE:** Critical paths used line up with critical paths given in original testbench

## Absolute Value Calculation

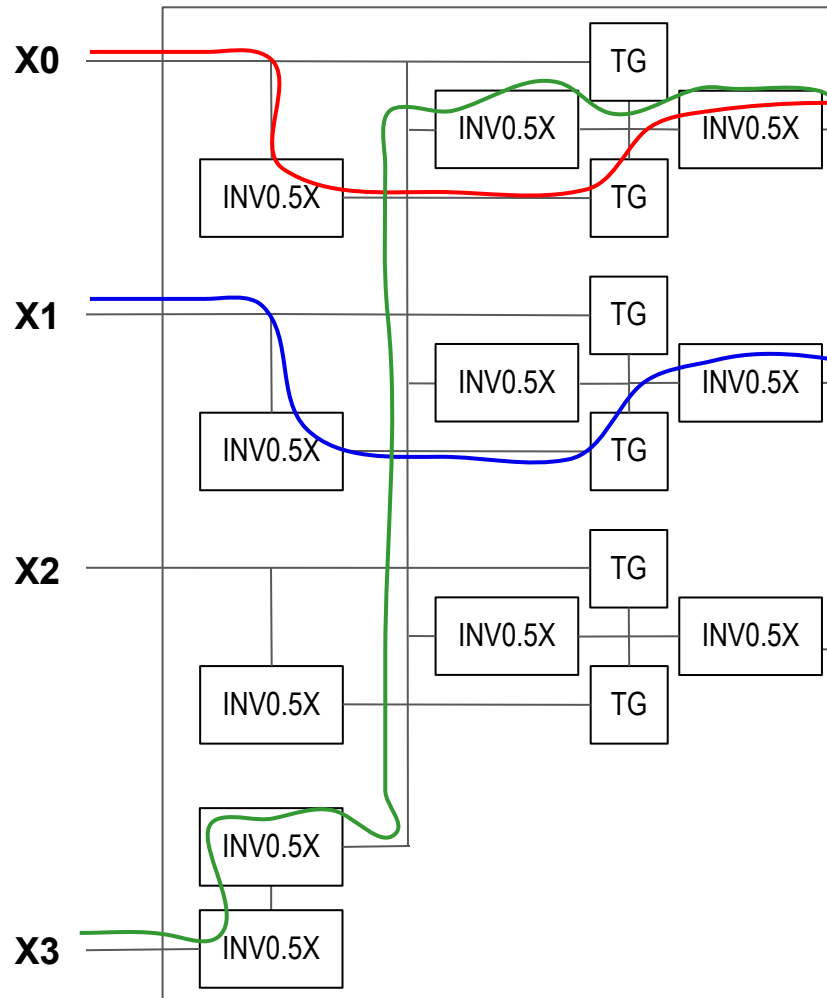

## Comparator

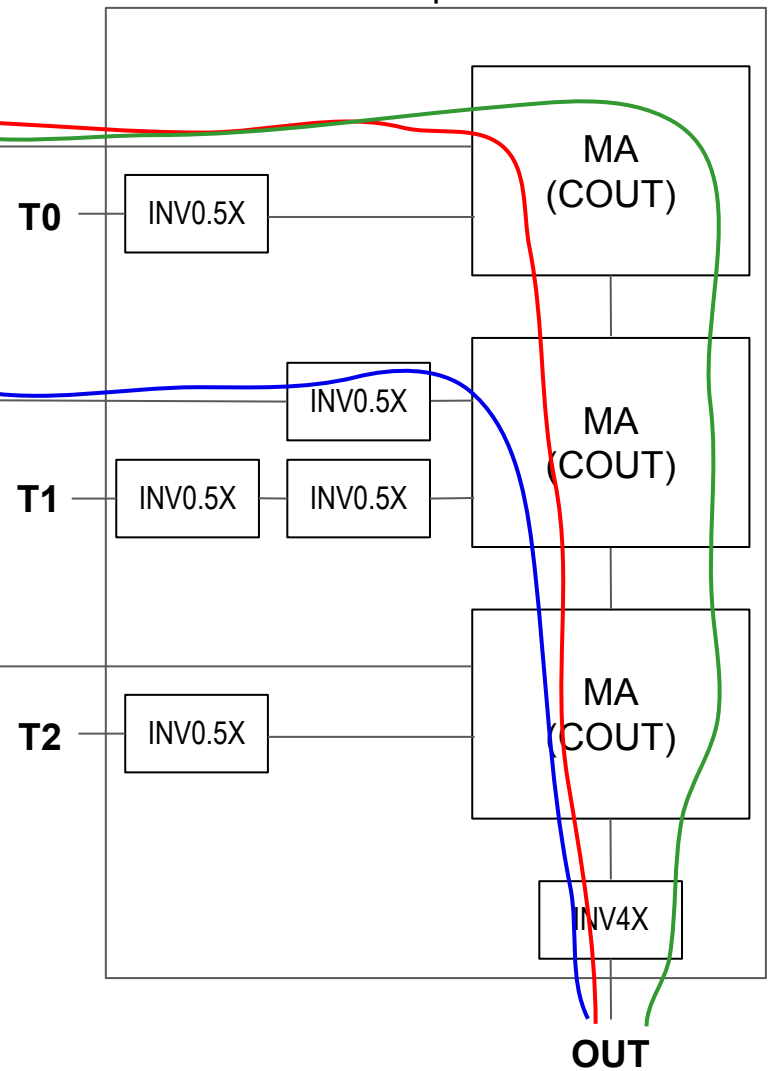

---

Schematic	Layout size	Energy	Verification
$V_{DD} = 571 \text{ mV}$ $t_{p\_X(0) \rightarrow OUT} = 685.2 \text{ ps}$ $t_{p\_X(1) \rightarrow OUT} = 663.4 \text{ ps}$ $t_{p\_X(2) \rightarrow OUT} = 570.9 \text{ ps}$	$X = 69.73 \text{ } \mu\text{m}$ $Y = 77.4 \text{ } \mu\text{m}$ $A = 5397.1 \text{ } \mu\text{m}^2$ Aspect Ratio = 1.11	Sch E = 119.3 fJ Layout E = 205.15 fJ $V_{DD-S} = 571 \text{ mV}$ $V_{DD-L} = 674 \text{ mV}$	Func: Y DRC: Y LVS: Y



# Most critical path: $X_0$ (Schematic)




$$V_{DD} = 1 \text{ V}$$




$$V_{DD} = 571 \text{ mV}$$

# Most critical path: $X_0$ (Layout)

 

$$V_{DD} = 1 \text{ V}$$

 


$$V_{DD} = 674 \text{ mV}$$

## 2<sup>nd</sup> most critical path: $X_1$ (Schematic)

---



$$V_{DD} = 1 \text{ V}$$

 

$$V_{DD} = 571 \text{ mV}$$

## 2<sup>nd</sup> most critical path: $X_1$ (Layout)

---




$$V_{DD} = 1 \text{ V}$$




$$V_{DD} = 674 \text{ mV}$$

# 3<sup>rd</sup> most critical path: $X_3$ (Schematic)

---

 


$$V_{DD} = 1 \text{ V}$$

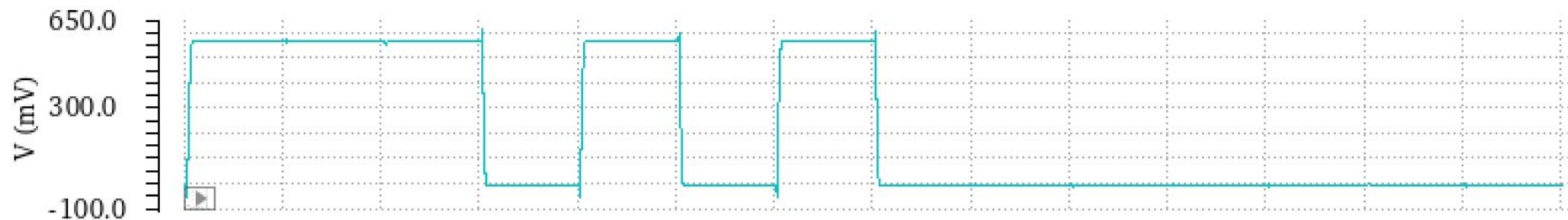

$$V_{DD} = 571 \text{ mV}$$
 
# 3<sup>rd</sup> most critical path: $X_3$ (Layout)




$$V_{DD} = 1 \text{ V}$$




$$V_{DD} = 674 \text{ mV}$$



# Output (Schematic)

 


$$V_{DD} = 1\text{ V}$$

 


$$V_{DD} = 571\text{ mV}$$

# Output (Layout)

 

$$V_{DD} = 1\text{ V}$$

 

$$V_{DD} = 674\text{ mV}$$

# Post-Layout Outputs for VDD = 1 V

The screenshot displays a circuit simulation software interface with three main panels:

- Design Variables:** A table with two rows: VDD (Value: 1) and VEXT (Value: 1).
- Analyses:** A table with two rows: tran (Type: transient, Enable: checked, Arguments: 0 70.1n moderate) and dc (Type: DC, Enable: checked, Arguments: t).
- Outputs:** A table with 20 rows, each representing a different output signal. The columns are Name/Signal/Expr, Value, Plot, Save, and Save Options.

The bottom status bar shows: Status: Ready | T=27 C | Simulator: spectre | State: spectre\_state1

Name	Value
1 VDD	1
2 VEXT	1

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 70.1n moderate
2 dc	<input checked="" type="checkbox"/>	t

Name/Signal/Expr	Value	Plot	Save	Save Options
1 X0		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
2 X1		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
3 X2		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
4 X3		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
5 OUT		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
6 V0/MINUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
7 V0/PLUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
8 tplh_X0_OUT	342.349p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
9 tphl_X0_OUT	334.424p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
10 tplh_X1_OUT	357.643p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
11 tphl_X1_OUT	348.783p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
12 tplh_X2_OUT	305.768p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
13 tphl_X2_OUT	293.549p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
14 tplh_X3_OUT	266.856p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
15 tphl_X3_OUT	353.578p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
16 Delay_X3_OUT	310.217p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
17 Delay_X2_OUT	299.659p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
18 Delay_X1_OUT	353.213p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
19 Delay_X0_OUT	338.386p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
20 Energy	485.411f	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

> Results in .../grad/deo/simulation/tb\_Abs\_Value\_Detector/spectre/config

5(8) Edit Variables ...

Status: Ready | T=27 C | Simulator: spectre | State: spectre\_state1

# Post-Layout Outputs for VDD = 674 mV

The screenshot displays a circuit simulation tool interface with three main panels: Design Variables, Analyses, and Outputs.

**Design Variables**

	Name	Value
1	VDD	674m
2	VEXT	674m

**Analyses**

	Type	Enable	Arguments
1	tran	<input checked="" type="checkbox"/>	0 70.1n moderate
2	dc	<input checked="" type="checkbox"/>	t

**Outputs**

	Name/Signal/Expr	Value	Plot	Save	Save
1	X0		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
2	X1		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
3	X2		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
4	X3		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
5	OUT		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
6	V0/MINUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
7	V0/PLUS		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
8	tpLh_X0_OUT	643.295p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
9	tpHl_X0_OUT	652.673p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
10	tpLh_X1_OUT	655.115p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
11	tpHl_X1_OUT	686.785p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
12	tpLh_X2_OUT	554.678p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
13	tpHl_X2_OUT	574.892p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
14	tpLh_X3_OUT	501.086p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
15	tpHl_X3_OUT	699.18p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
16	Delay_X3_OUT	600.133p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
17	Delay_X2_OUT	564.785p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
18	Delay_X1_OUT	670.95p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
19	Delay_X0_OUT	647.984p	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
20	Energy	205.147f	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

Plot after simulation: **Auto** Plotting mode: **Replace**

14(25) Choose Design ... Status: Ready | T=27 C | Simulator: spectre | State: spectre\_state1

# Delay and Energy

Schematic		Layout	
$V_{DD} = 1\text{ V}$ $E = 403.12\text{ fJ}$	$V_{DD} = 571\text{ mV}$ $E = 119.3\text{ fJ}$	$V_{DD} = 1\text{ V}$ $E = 485.41\text{ fJ}$	$V_{DD} = 674\text{ mV}$ $E = 205.15\text{ fJ}$
$t_{p\_X(0) \rightarrow OUT} = 244.3\text{ ps}$ $t_{plh\_X(0) \rightarrow OUT} = 246.5\text{ ps}$ $t_{phl\_X(0) \rightarrow OUT} = 242.0\text{ ps}$  $t_{p\_X(1) \rightarrow OUT} = 240.4\text{ ps}$ $t_{plh\_X(1) \rightarrow OUT} = 243.9\text{ ps}$ $t_{phl\_X(1) \rightarrow OUT} = 236.9\text{ ps}$  $t_{p\_X(3) \rightarrow OUT} = 203.3\text{ ps}$ $t_{plh\_X(3) \rightarrow OUT} = 174.1\text{ ps}$ $t_{phl\_X(3) \rightarrow OUT} = 232.5\text{ ps}$	$t_{p\_X(0) \rightarrow OUT} = 685.2\text{ ps}$ $t_{plh\_X(0) \rightarrow OUT} = 670.5\text{ ps}$ $t_{phl\_X(0) \rightarrow OUT} = 699.9\text{ ps}$  $t_{p\_X(1) \rightarrow OUT} = 663.4\text{ ps}$ $t_{plh\_X(1) \rightarrow OUT} = 637.6\text{ ps}$ $t_{phl\_X(1) \rightarrow OUT} = 689.2\text{ ps}$  $t_{p\_X(3) \rightarrow OUT} = 570.9\text{ ps}$ $t_{plh\_X(3) \rightarrow OUT} = 463.3\text{ ps}$ $t_{phl\_X(3) \rightarrow OUT} = 678.5\text{ ps}$	$t_{p\_X(0) \rightarrow OUT} = 338.4\text{ ps}$ $t_{plh\_X(0) \rightarrow OUT} = 342.3\text{ ps}$ $t_{phl\_X(0) \rightarrow OUT} = 334.4\text{ ps}$  $t_{p\_X(1) \rightarrow OUT} = 353.2\text{ ps}$ $t_{plh\_X(1) \rightarrow OUT} = 357.6\text{ ps}$ $t_{phl\_X(1) \rightarrow OUT} = 348.8\text{ ps}$  $t_{p\_X(3) \rightarrow OUT} = 310.2\text{ ps}$ $t_{plh\_X(3) \rightarrow OUT} = 266.9\text{ ps}$ $t_{phl\_X(3) \rightarrow OUT} = 353.6\text{ ps}$	$t_{p\_X(0) \rightarrow OUT} = 648.0\text{ ps}$ $t_{plh\_X(0) \rightarrow OUT} = 643.3\text{ ps}$ $t_{phl\_X(0) \rightarrow OUT} = 652.7\text{ ps}$  $t_{p\_X(1) \rightarrow OUT} = 671.0\text{ ps}$ $t_{plh\_X(1) \rightarrow OUT} = 655.1\text{ ps}$ $t_{phl\_X(1) \rightarrow OUT} = 686.8\text{ ps}$  $t_{p\_X(3) \rightarrow OUT} = 600.1\text{ ps}$ $t_{plh\_X(3) \rightarrow OUT} = 501.1\text{ ps}$ $t_{phl\_X(3) \rightarrow OUT} = 699.2\text{ ps}$

---

# Discussion